



Lab 1 - Logic Gates Pandemic Edition

Copyright © 2007-2021, Jesus Calvino-Fraga. Not to be copied, used, or revised without explicit written permission from the copyright owner.


In this laboratory you will implement a simple digital system using logic gates built with discrete transistors.

Tools and Parts Needed

Due to the pandemic, this laboratory experiment will be completed using NI Multisim only. So we don't need any tools or parts.

Activities

 - 1) The diagram below shows a basic DTL 2-input NAND gate. Test the gate using Multisim and verify that it operates as expected.



- 2) Add the last two digits of your student number. From the result pick the four digits from the table below.

Sum	Display	Sum	Display
0	0523	10	3946
1	2038	11	2386
2	5261	12	7951
3	4386	13	5379
4	4826	14	2508
5	1268	15	2159
6	7480	16	3527
7	3274	17	9630
8	6321	18	8316
9	1625		

Design and simulate with Multisim a 2-bit decoder that displays the digits that correspond to your student number using a 7-segment common anode display as indicated in the table below. Remember that the LED segments are turned on with logic 0. Use ONLY DTL NAND logic gates (with any number of inputs; a 'NAND' gate with only one input is a valid option!).

Inputs		Digits (left to right)
B	A	
0	0	Digit 1
0	1	Digit 2
1	0	Digit 3
1	1	Digit 4

For example, if the last two digits of your student number add up to decimal 14, then you have to display "2508" with the 7-segment display. When the binary input is 00 display number 2, when the binary input is 01 display 5, when the binary input is 10 display 0, and when the binary input is 11 display 8.

To build your decoder you are limited to the following maximum number of components:

1. Up to 8 NPN transistors
2. Up to 24 diodes
3. Up to 16 resistors

The current limiting resistors for the 7-segment display are not included in the limitations above. Push buttons or switches used to control the inputs are also not included in the limitations above.

Upload to canvas you Multisim files (one for the DTL gate test, and one for the decoder) and a PDF with the complete design process of your decoder.